
## Smart Power Efficient Light Automated System


Team Glow Rishi, Vamshi, Harshvardhan, Satyam

#### **Problem Statement:**


Smart Selection of Most Power Efficient Combination of light devices present in a room at the place of operation based on Idr sensor detection and requirement of user(different modes like sleep, study,etc),optimising solution by analyzing RMS AC Voltage Power Variation Curve

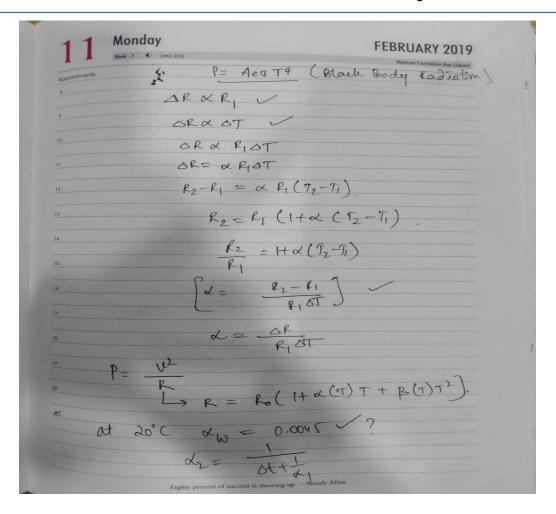
# Mathematics of Power-Voltage Curve Optimization



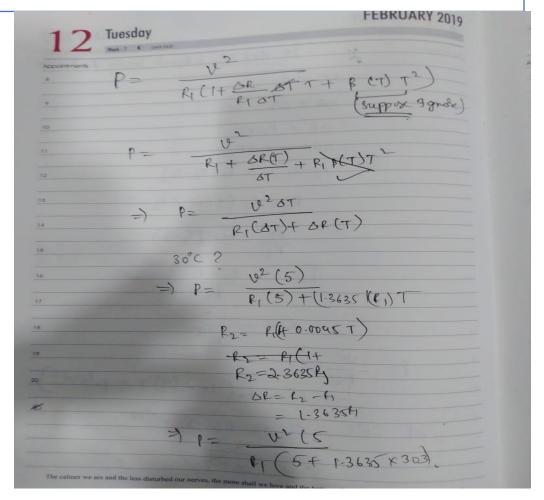

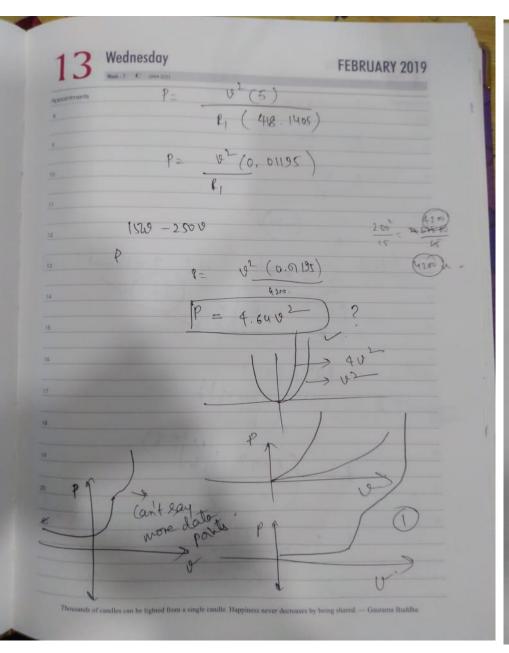 We are basically trying to optimize power consumption by selecting the combination of light devices which has minimum power voltage gradient so as to maximize o/p from given input with low consumption of power




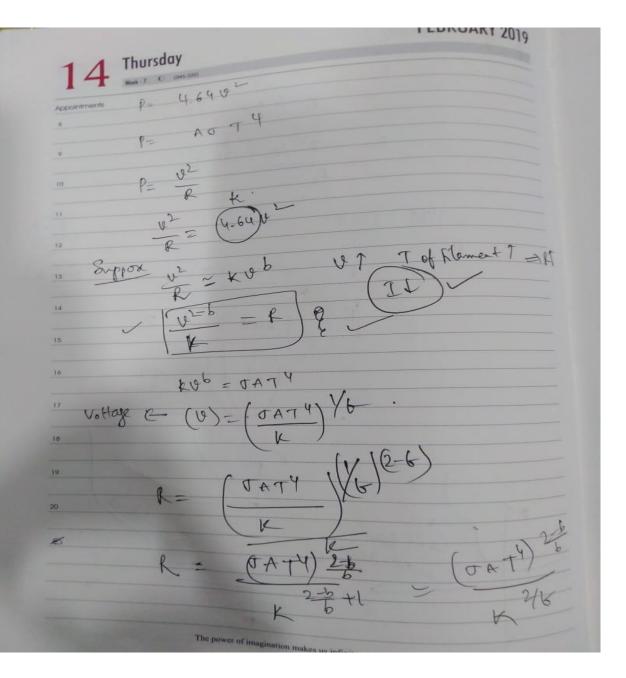


FEBRUARY 2019 Friday - a regative dependence. so we cart actually predict behaviour of an function — 150 many date People often say that motivation doesn't last. Well, neither does bathing. That's why we recommend it daily. —Zig Ziglar
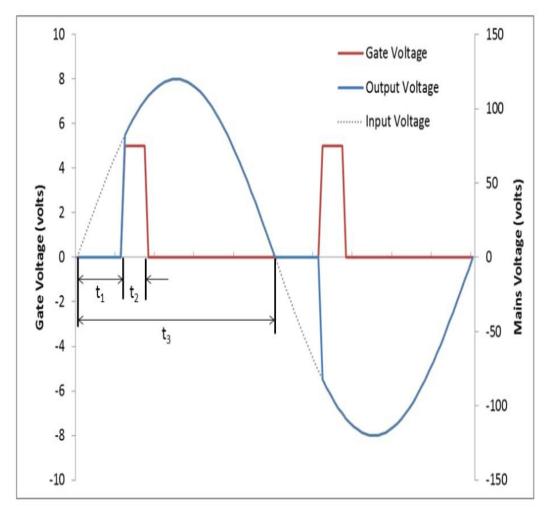
#### Components

- Arduino board
- BT136 Triac
- 220V AC lamp
- LM339 comparator
- Optocoupler (MOC3021)
- 2 x 1N4007 diode (or 1N4001)
- LDRs




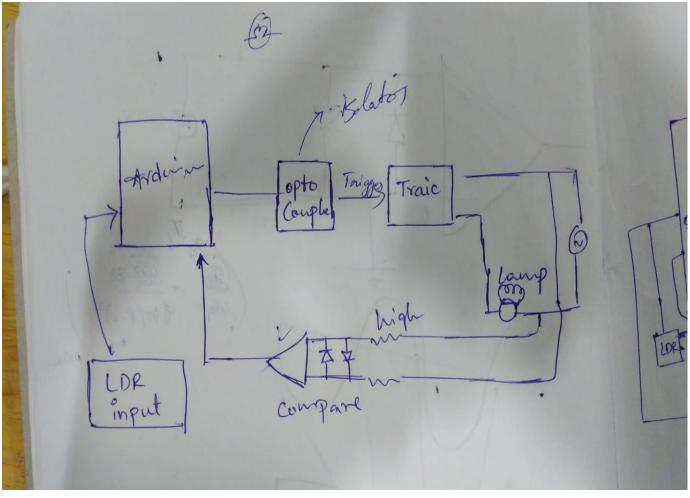


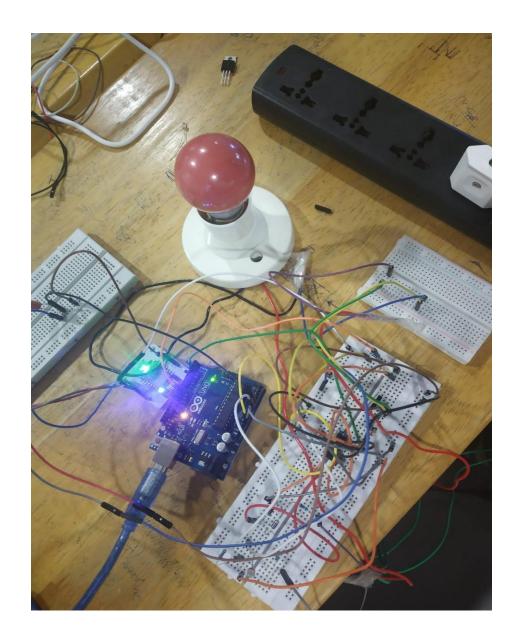
#### Code

```
#define triac_gate 8
#define pot A0
#define iot A1
                                     Ã0
A1
  int ldr=0;
 int app=0;
bool ZC = 0;
 uint16_t alpha;
int value=0;
 void setup(void) {
  pinMode(triac_gate, OUTPUT);
  digitalWrite(triac_gate, LOW);
  attachInterrupt(0, ZC_detect, CHANGE);
                                                                                                        // Enable external interrupt (INTO)
 void ZC_detect() {
  ZC = 1;
 void loop() {
   if( ZC){
  if(alpha < 9500) {
    delayMicroseconds(alpha);
    digitalWrite(triac_gate, HIGH);
    delayMicroseconds(200);
    digitalWrite(triac_gate, LOW);
}</pre>
```

```
ZC = 0;
  ldr=analogRead(pot);
app=analogRead(iot);
if(app<60)
{alpha=9000;</pre>
  else if(app>660)
{alpha=2000;
   else if(app>140 && app<270)//sleep { if(ldr<780)
     alpha=alpha+1;
else if(ldr>830)
     alpha=alpha-1;
else
     {alpha=map(ldr,0,680,9600,0); if(alpha > 9500)
      alpha = 9500;
   else if(app>320 && app<440)//study { if(ldr<920) alpha=alpha+1; else if(ldr>980)
     alpha=alpha-1;
else
     {alpha=map(ldr,0,680,9600,0); if(alpha > 9500)
      alpha = 9500;
   if(alpha > 9500)
   alpha = 9500;
else if (alpha<0)
   alpha=0;
```



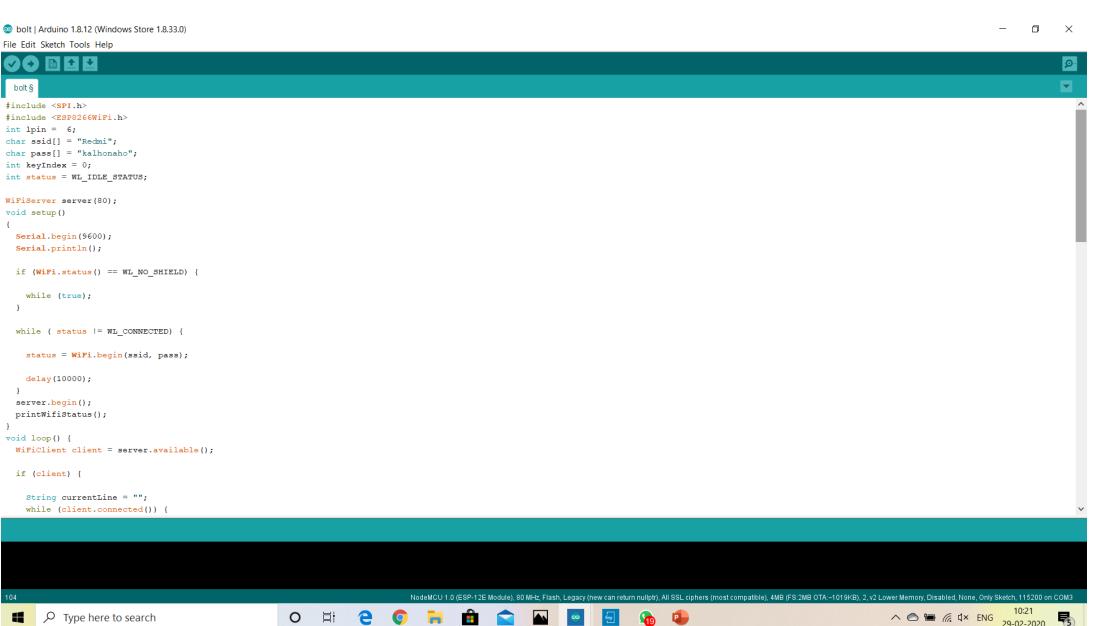

 



















 





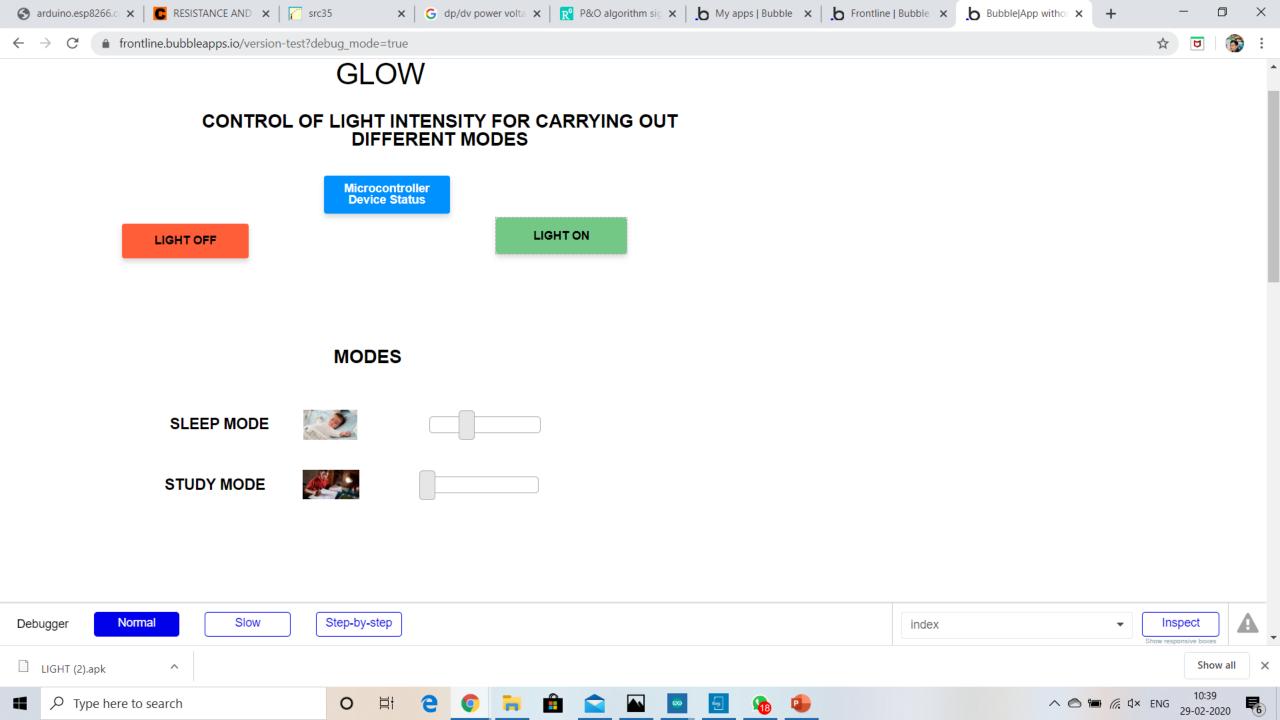

### Circuit Implementation

